
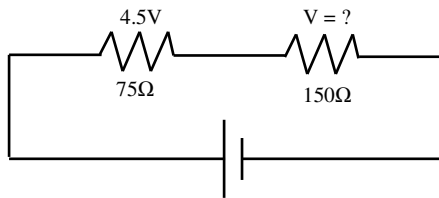


1. After working the circuit at the right (meaning do all your work on the diagram first), answer the following.


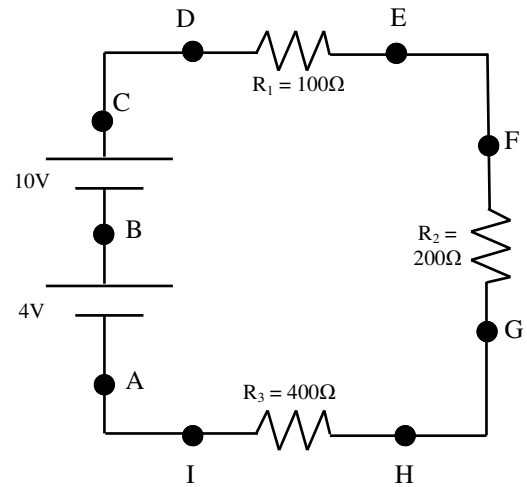
- A. * Calculate the current flowing thru the circuit?
- B. If one of the resistors is replaced by a wire, how will the current change (increase, decrease, stay the same)?
- C. If a third battery is added to the circuit, how will the current change?
- D. How much current is flowing thru the 100Ω resistor?
- E. * How much voltage is used by the 100Ω resistor?
- F. * How much power is used by the 100Ω resistor?
- G. Calculate how much voltage is left at point E.
- H. * On the diagram, calculate the voltage used by the other two resistors.
- I. How does the voltage drop across R_1 compare with R_2 ?
- J. How does the resistance of R_1 compare with R_2 ?
- K. How does the voltage drop across R_2 compare with R_3 ?
- L. How does the resistance of R_2 compare with R_3 ?
- M. Using the V_{total} and I_{total} , calculate P_{total} for the whole circuit.





- 2. Now, using what you learned from parts I-L above (and the lab),
 - A. How much voltage is used by the 150Ω ?
 - B. What is the voltage of the battery?
 - C. * How much current is flowing (in mA)?

3. AC or DC Current?

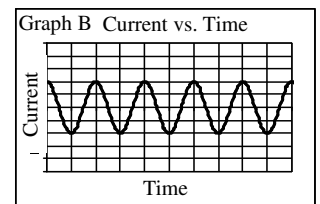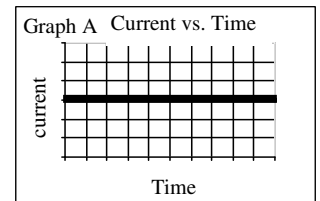- A. ___ * Current that changes polarity.
- B. ___ Current that is constant.
- C. ___ What comes from a battery.
- D. ___ What comes from the power outlet.
- E. ___ Graph A at the right.
- F. ___ Graph B.




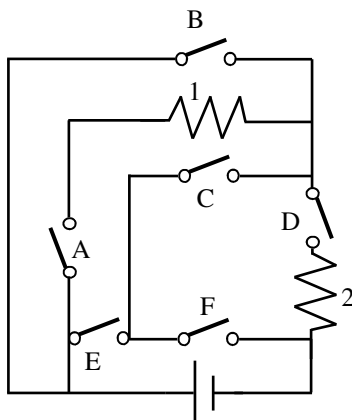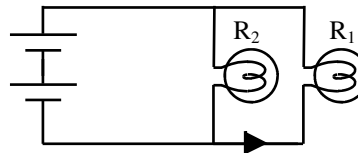4. In the circuit at the right, R_1 isn't working. Without doing anything to the light bulbs, what is one change that would make R_1 turn on?



- 5. In the diagram at the right you will need to decide which switches to close to allow different situations. Start at the + side of the battery (the big side). This is like maze games—follow the path, but be sure you don't make a short-circuit. Which resistor or resistors allows:
 - A) * only resistor 1 to have current in it?
 - B) only resistor 2 to have current thru it?
 - C) to by-pass both resistors?
 - D) for electricity to go thru both resistors?

(Review Question on back)

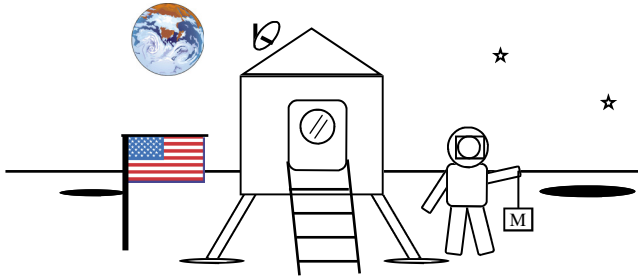

6. Slim Jim is also an astronaut. The acceleration due to gravity on the moon is 1.63 m/s^2 . Jim is lifting a 18 kg object from the ground with a rope.
- * What is the weight of the object on the moon?
 - Draw a force body diagram (FBD) for the mass (below the picture).
 - If Jim can pull upward with a force of 450N , calculate the acceleration of the mass.
 - If the radius of the moon is $1.74 \times 10^6 \text{ m}$, calculate the mass of the moon. (*You have the force of gravity due to the moon and the mass of object 1.*)

1A: 0.02 A (which is 20 mA)

1E: $V = IR = .02(100) = 2\text{V}$

1F: $P = VI$ or $= I^2R = 0.04\text{W}$

1H: $V_2 = 4\text{V}$ $V_3 = 8\text{V}$

2C: You have the voltage and resistance of one resistor, calculate the current. And since it is a series circuit, isn't that the total?

3A: AC

5A: Switches: A, C, and D. You can't have D on or R2 comes on. You can't have E on or it will bypass R1 completely with a short circuit.

6A: Come on: $F_w = mg$ this g just isn't 9.8 m/s^2 .