
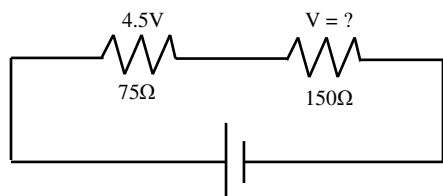


1. After working the circuit at the right, answer the following.

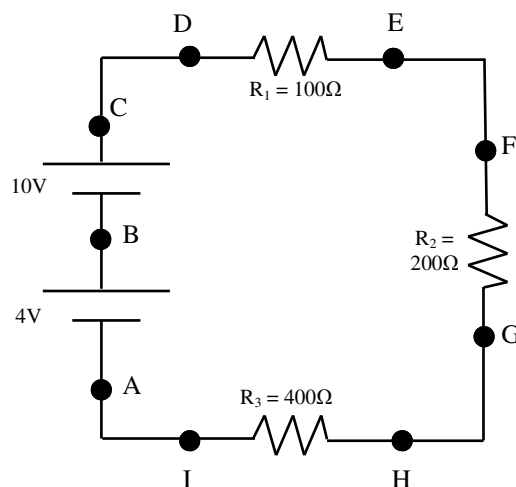- A. Calculate the current flowing thru the circuit.
- B. If one of the resistors is replaced by a wire, how will the current change?
- C. If a third battery is added to the circuit, how will the current change?
- D. How much current is flowing thru the  $100\Omega$  resistor?
- E. How much voltage is used by the  $100\Omega$  resistor?
- F. How much power is used by the  $100\Omega$  resistor?
- G. Calculate how much voltage is left at point E.
- H. On the diagram, calculate the voltage used by the other two resistors.
- I. How does the voltage drop across  $R_1$  compare with  $R_2$ ?
- J. How does the resistance of  $R_1$  compare with  $R_2$ ?
- K. How does the voltage drop across  $R_2$  compare with  $R_3$ ?
- L. How does the resistance of  $R_2$  compare with  $R_3$ ?
- M. Calculate the power used by the other two resistors
- N. How much power does the whole circuit use?



2. Now, using what you learned from parts I-L above,

- A. How much voltage is used by the  $150\Omega$ ?
- B. What is the voltage of the battery?
- C. How much current is flowing?



3. Series or parallel? (Using your lab notes or the "Types of Circuits" notes)

- |   |  |
|---|--|
| A. ___ Only one path for the electricity to flow.                 | E. ___ If one light turns off, the others stay on.         |
| B. ___ Paths are dependent on each other (one affects the other). | F. ___ If you turn off one light, all the lights turn off. |
| C. ___ How your house is wired.                                   | G. ___ Has more than one path for the electricity to flow. |
| D. ___ Paths are independent of each other.                       | H. ___ Two devices have the same current.                  |
|   | I. ___ Two devices have the same voltage.                  |

4. The holes at the right are pipes.

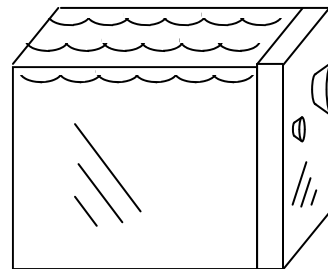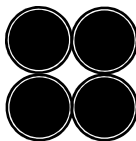- A. Are the four holes in parallel or series, as shown?
- B. Together is there a bigger hole or a smaller hole for water to flow thru?
- C. Each pipe can allow 2 gal/sec, how much can flow thru them together?
- D. So, is the resistance increasing or decreasing?

*This is why 4 equal resistors in parallel are the same as a single resistor that is 1/4th as big.*







5. Five  $100\Omega$  resistors are placed in a circuit.

- A. What is the total resistance if they are in series?
- B. What is the total resistance if they are in parallel?

6. Imagine a large tank of water. In one side of the tank are two holes with plugs in them: a large hole and a small hole.

- A. When removed, which hole will have more resistance?
- B. Which hole will have more water flowing (current) thru it?
- C. Water, like electricity, always takes the path of:

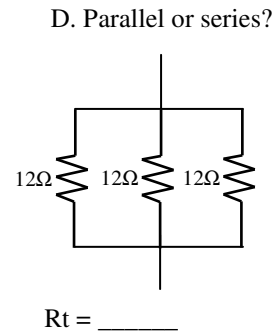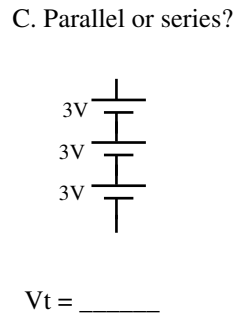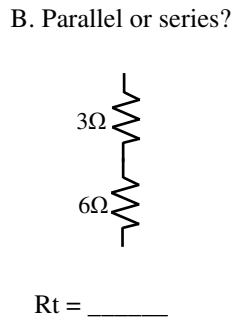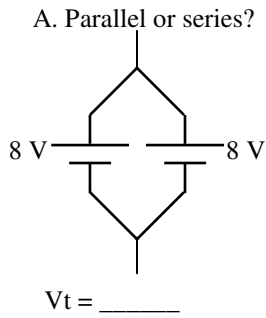7. Decide if the following are in parallel or series and find the total voltage or total resistance. (See “Types of Circuits”)



8. AC or DC Current?

- |                                       |  |
|---------------------------------------|--|
| A. ___ Current that changes polarity. | D. ___ What comes from the power outlet. |
| B. ___ Current that is constant.      | E. ___ Graph A                           |
| C. ___ What comes from a battery.     | F. ___ Graph B.                          |



9. How long does it take for a 6 volt battery to push 12 coulombs thru a 960Ω resistor?

10. In a circuit, the resistance doubles and the voltage is halved. How does the power change?

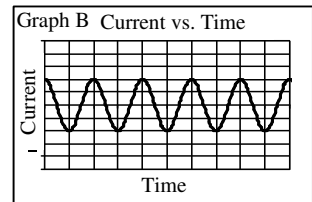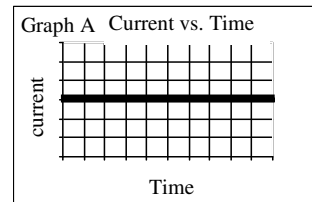11. A vacuum cleaner pulls 12A when hooked up to a 120V wall outlet.


A person uses the vacuum 30 minutes a day every day for 2 weeks.

- How much power does it use?
- How many hours is it run?
- How many kWhrs, were used?
- If the power company charges 11 cents per kWhr, how much did this cost?



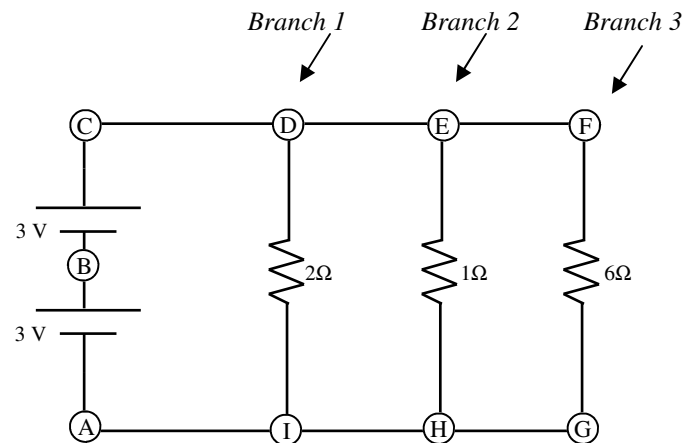
12. Use the circuit at the right to answer the following.

- If the 6Ω resistor is disconnected,
  - how will it affect the current in the 2Ω resistor?
  - how will the total current change?
  - how will the total resistance change?
- What is the voltage at point H?
- What is the voltage at point F?
- What is the voltage from point E to point H?
- Calculate the current in each branch.
- Which resistor has the most voltage across it?
- Which resistor has the most current running thru it?
- What is the current flowing from H to I?
- What is the total current of the circuit?
- How much power is used by the 6Ω resistor?
- Calculate the total resistance of the circuit.
- Calculate the power dissipated by the 1Ω resistor.



- Calculate the power dissipated by the 6Ω resistor.
- How much power is used by the entire circuit?

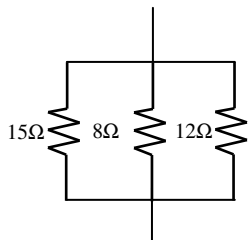13. Calculate the total resistance of the resistors shown.



### Resistors in Parallel


$$\frac{1}{R_{total}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \dots$$

### Resistors in Series

$$R_{total} = R_1 + R_2 + R_3 \dots$$

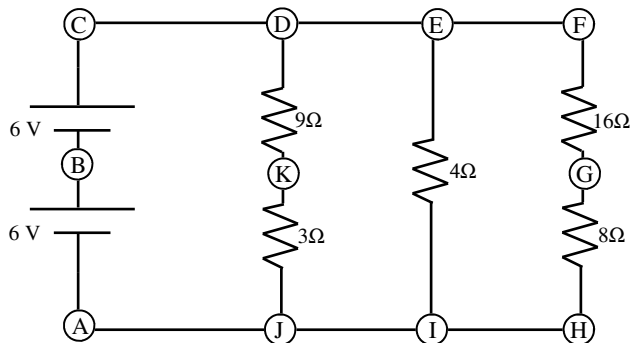14. After working the circuit, answer the following.

- What is the total resistance of branch 1  
(write this at K)?
- What is the current flowing thru branch 1?
- What is the current flowing thru the 9Ω?
- How much voltage does the 9Ω use?
- How much current flows thru the 4Ω?
- What is the total resistance of branch 3  
(write this at G)?
- What is the current flowing thru the 16Ω?
- How much voltage does the 16Ω use?
- How much voltage is left at point G?
- How much charge passes thru the 16Ω each minute?
- How much current flows from I to J?
- What is the total current of the circuit?
- Using the total current and voltage, calculate the total resistance of the circuit.
- Using the total resistances of the branches (4Ω and what's at K and G), calculate the total resistance of the circuit.
- Calculate the total power of the circuit.
- How much energy does the circuit use in 20 seconds?




Transcription:	Process in which DNA is copied into mRNA. ( <i>Before it can <u>ride</u> it must transcribe.</i> )
Translation:	Process in which proteins are made from tRNA. ( <i>Before it can <u>create</u> it must translate.</i> )
Ribosomes:	Cell organelle where proteins are created.
Amino Acids:	Building blocks of proteins.
Codon:	Three base code that tells the ribosome what amino acid to make. Ex. AGA

15. Translation (TL) or Transcription (TS)?

- A. \_\_\_\_ When mRNA is turned into tRNA.
- B. \_\_\_\_ When DNA is turned into mRNA.
- C. \_\_\_\_ Occurs in the nucleus.
- D. \_\_\_\_ Occurs at the ribosomes.

16. The three nitrogen base code that tells the r\_\_\_\_\_ which a\_\_\_\_\_ a\_\_\_\_\_ to make is called a:

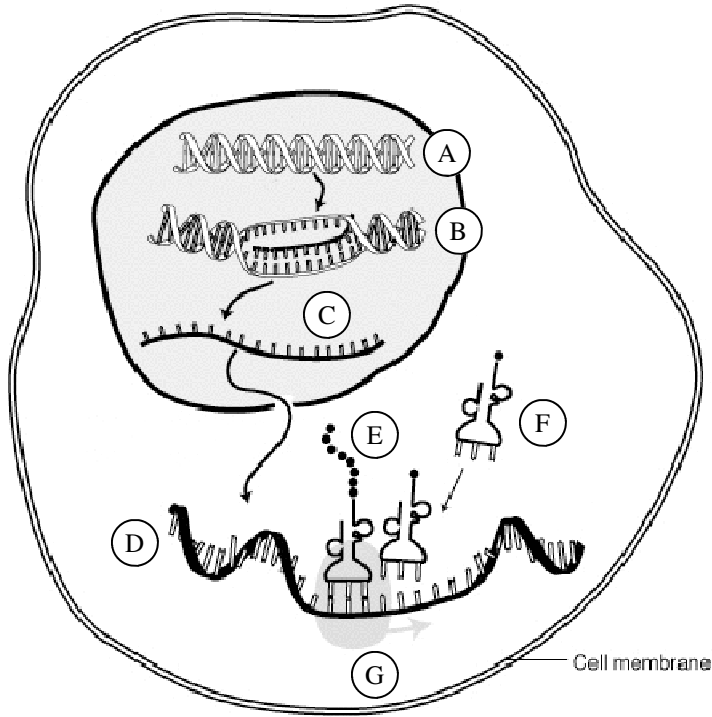17. The picture at the left shows the steps in protein synthesis in an animal cell.



- A. The double coiled molecule at letter A is called the \_\_\_\_\_.
- B. The double coiled molecule is unzipping and giving its code to the single stranded molecule at letter B. This single stranded molecule is the \_\_\_\_\_.
- C. The process in which molecule A becomes molecule C is called t\_\_\_\_\_.
- D. Molecule F is called the \_\_\_\_\_.
- E. When D becomes F is called t\_\_\_\_\_.
- F. Letter E shows the chaining of amino acids to make a p\_\_\_\_\_.
- G. Two of the major organelles are shown in grey.
  - i. A, B, and C are in the \_\_\_\_\_.
  - ii. G shows the \_\_\_\_\_.

18. From the codon chart below, what amino acid comes from the codon: CAG?

Second Nitrogen Base (2nd letter)

		Second Nitrogen Base (2nd letter)								
		U		C		A		G		
First Nitrogen Base (1st letter)	U	UUU	Phenylalanine	UCU	Serine	UAU	Tyrosine	UGU	Cysteine	U
		UUC		UCC		UAC		UGC		C
		UUA	Leucine	UCA		UAA	Ochre	UGA	Opal	A
		UUG		UCG		UAG	Amber	UGG	Tryptophan	G
	C	CUU	Leucine	CCU	Proline	CAU	Histidine	CGU	Arginine	U
		CUC		CCC		CAC		CGC		C
		CUA		CCA		CAA	CGA	A		
		CUG		CCG		CAG	CGG	G		
	A	AUU	Isoleucine	ACU	Threonine	AAU	Asparagine	AGU	Serine	U
		AUC		ACC		AAC		AGC		C
		AUA	ACA	AAA		Lysine	AGA	Arginine	A	
		AUG	Methionine	ACG			AAG		AGG	G
	G	GUU	Alanine	GCU	Alanine	GAU	Aspartic acid	GGU	Glycine	U
		GUC		GCC		GAC		GGC		C
		GUA		GCA		GAA	Glutamic acid	GGA		A
		GUG		GCG		GAG		GGG		G